



# Introduction To SPICE



## Outline





### Introduction

- Value of Prototyping
- Analog Simulation
- Where To Get Spice
- Summary



# Open-Loop Design

Design  
Specs  
&  
Methods

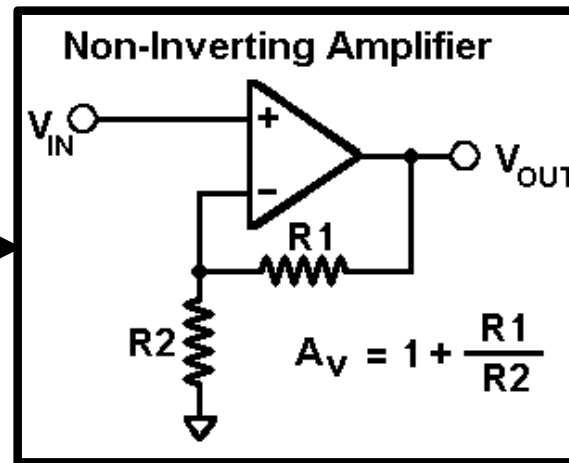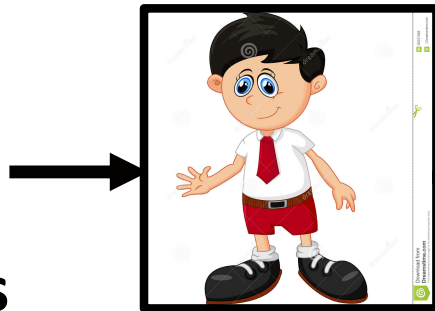


Circuit  
Schematic

- How does the student know the design methods lead to a workable solution?
- How does the student know the Professor knows what he talking about?



# Spice Will Help Close The Loop

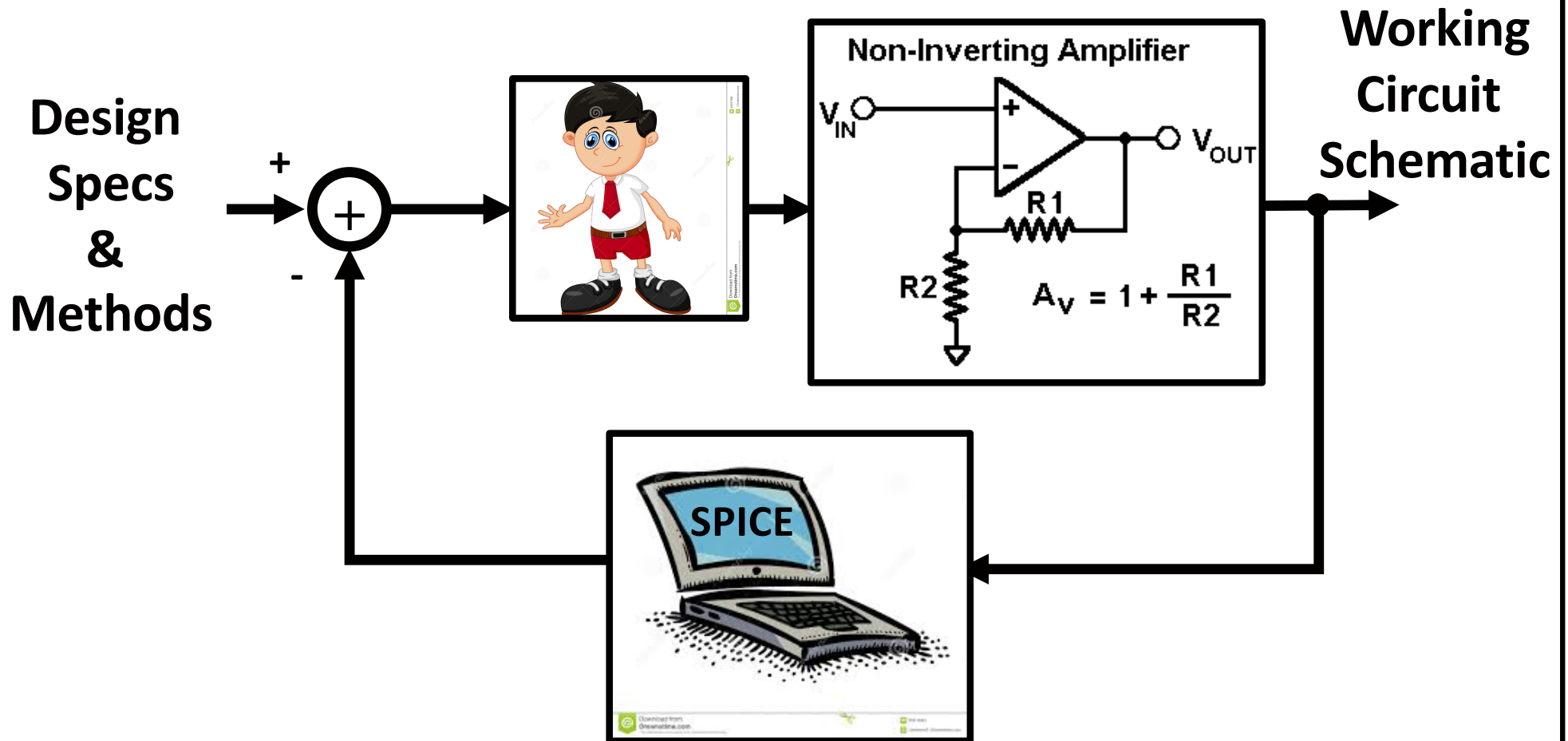




## Outline

- Introduction
- ➡ Value of Prototyping
- Analog Simulation
- Where To Get Spice
- Summary




# Sidetone Generator Circuit

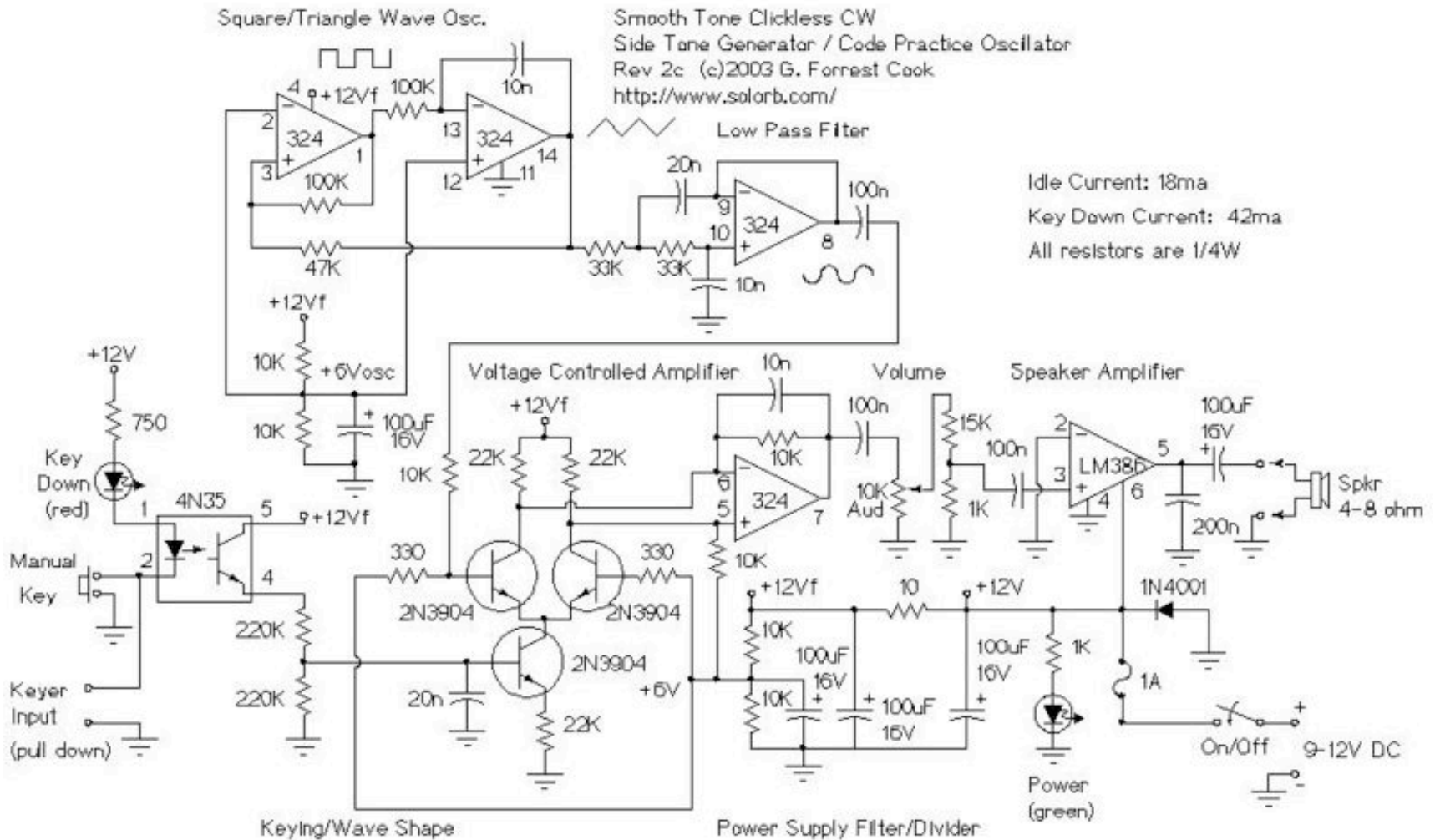




# Prototyping Electronic Circuit

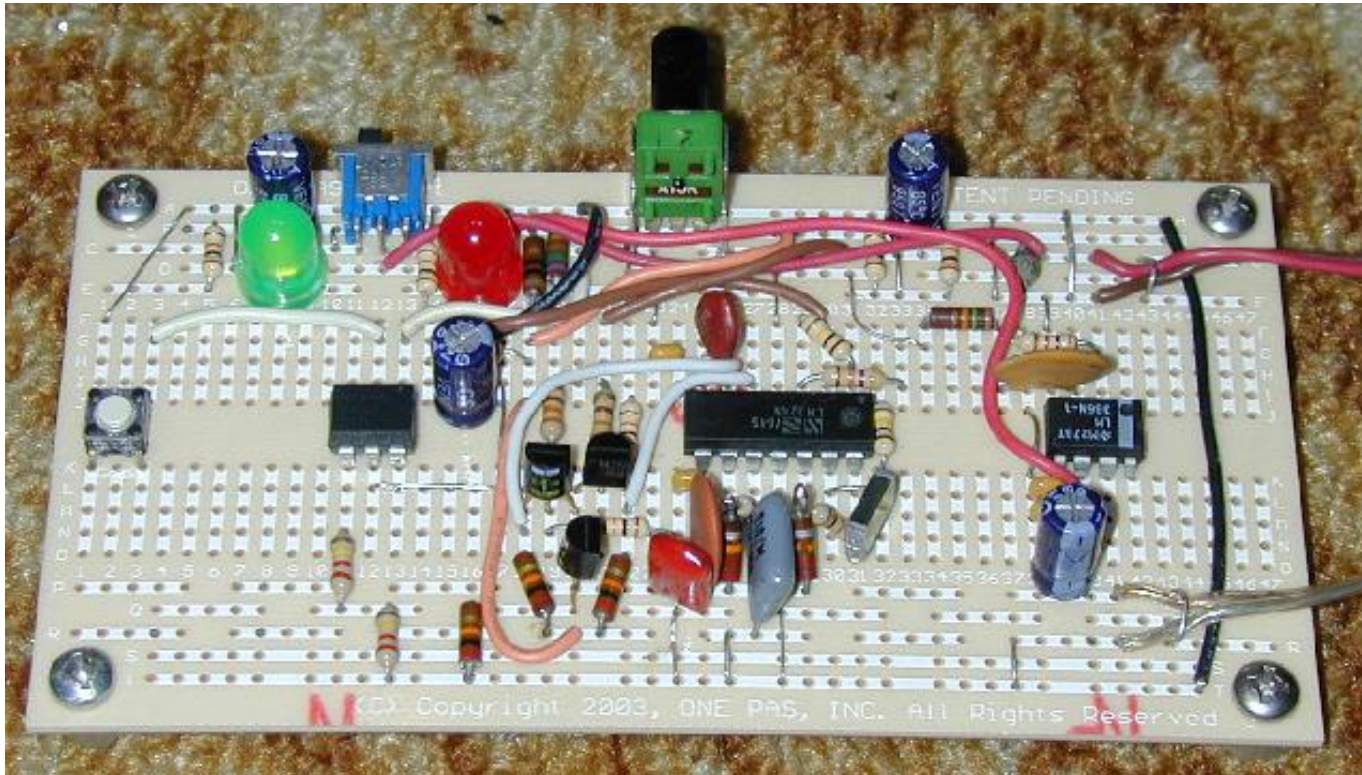

- To verify that your design works correctly, a prototype of the circuit is constructed.





# Laboratory Bench Setup

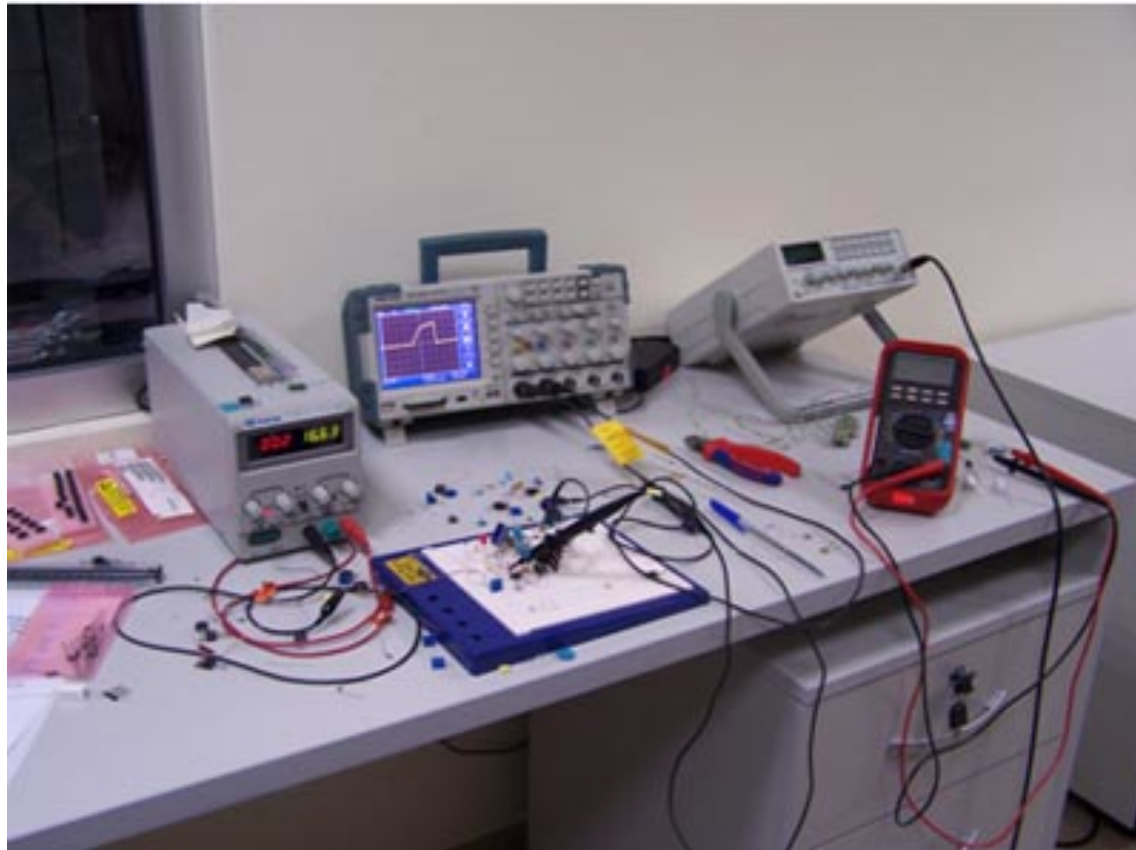

- Engineer will characterize design using a set of signal generators and measuring instruments.



# Mass Production

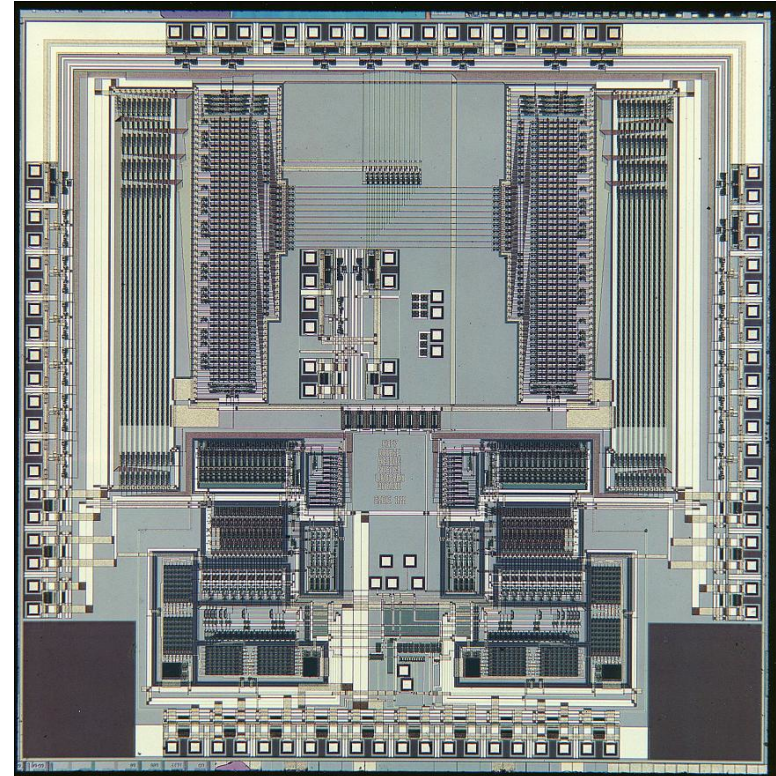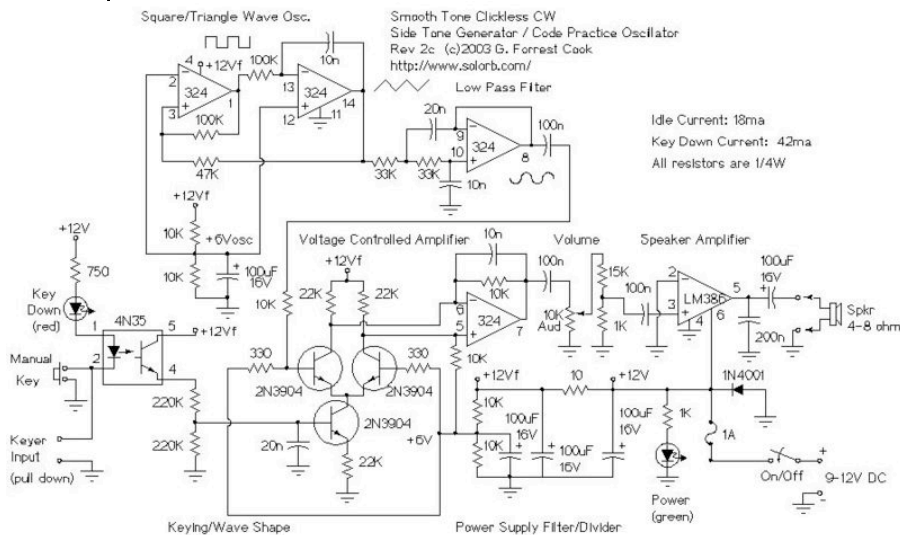

- IC Implementation (1 cm x 1 cm dimensions) when volumes are high and small size is required.



## Time And Money

- All this activity takes time.
- Engineering principle:
  - ***Every successful project takes at least two iterations to get it right.***
- Investors want ROI (Return On Investment) in near zero time.
  - Calls for innovative solutions.
    - » Electronic Engineers responded with the idea of a circuit simulator.
      - improves design times and reduces engineering errors (get it right the first time).



## Outline

- Introduction
- Value of Prototyping
- ➡ Analog Simulation
- Where To Get Spice
- Summary



# Analog Circuit Simulation

- **SPICE** - Simulation Program with Integrated Circuit Emphasis
  - developed at University of California/Berkeley
  - coincided with emergence of “Silicon Valley” across the “bay”
  - widely adopted, *de facto* standard.
- Numerical approach to circuit simulation (as opposed to symbolic)
  - circuit nodes/connections define a matrix
  - external nodes provide boundary conditions.
- Circuit elements represented by device models
  - simple (eg., resistor)    - complex (eg. MOSFET)



# Types of Analysis

- Three basic analysis available:
  - **DC Analysis**
    - » calculates DC voltages and currents in a circuit (nonlinear)
    - » Also referred to as DC bias or operating point
  - **Transient Analysis**
    - » calculates the behavior of a circuit subject to time-varying input signals.
    - » most important analysis but very time consuming
  - **AC Analysis**
    - » Small-signal or linear analysis
    - » Take care when using this command, as amplitude of input signal has no significance.



## Other Analysis Types

- Special case of the previous three:
  - **DC sweep, transfer function (TF) and temperature.**
    - » Repeated use of DC Analysis
  - **Fourier and Monte Carlo analysis.**
    - » Post-processing of results from Transient Analysis
  - **Noise and robustness analysis**
    - » Post-processing of results from AC Analysis




## Transient Analysis

- Most important analysis, but most time consuming and riddled with convergence problems
  - failure to converge due to missing connection
  - time step too small due to rise and fall times
- Many of today's circuits are difficult to analyze with SPICE due to widely varying time constants (poles spread very far apart).
  - long simulation times required.
- Nonetheless, circuit simulation is here to stay; all engineering disciplines use some form of computer-based simulation.



# Input /Output To SPICE

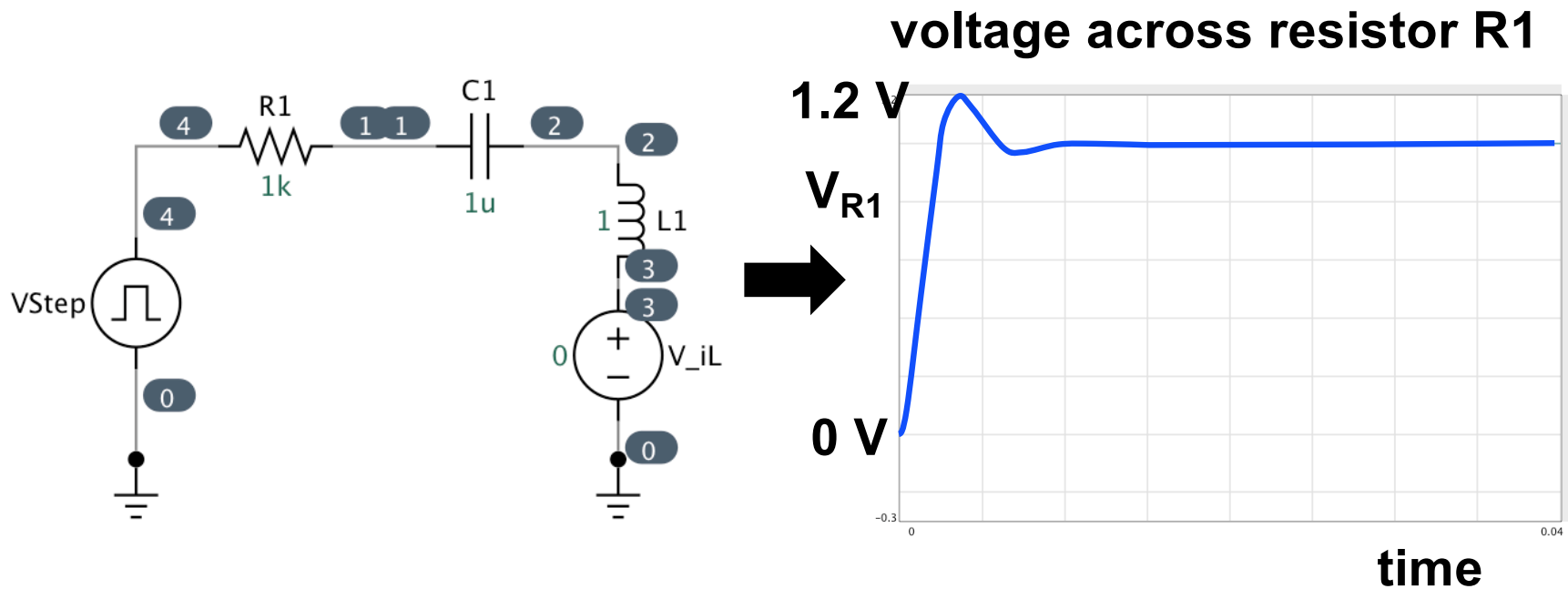



# Spice Description Language: Passive Elements



## Passive Elements

<u>Element</u>	<u>Spice Description</u>
	<code>Rname n+ n- value</code>
	<code>Cname n+ n- value [ IC=initial_voltage_condition ]</code>
	<code>Lname n+ n- value [ IC=initial_current_condition ]</code>

**Figure 1.4** Spice descriptors for passive elements. Fields surrounded by [ ] are optional.


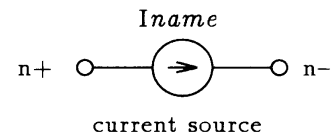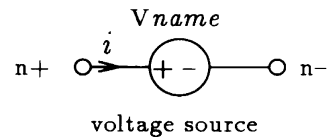
# Spice Description Language: Independent Sources



## Spice Description

## Type Of Analysis




$\begin{Bmatrix} Vname \\ Iname \end{Bmatrix}$	$n+ \ n- \text{ DC value}$	All Types
$\begin{Bmatrix} Vname \\ Iname \end{Bmatrix}$	$n+ \ n- \text{ AC magnitude phase\_degrees}$	AC Frequency Response
$\begin{Bmatrix} Vname \\ Iname \end{Bmatrix}$	$n+ \ n- \text{ SIN } ( V_o \ V_a \ freq \ t_d \ damp )$	Transient
$\begin{Bmatrix} Vname \\ Iname \end{Bmatrix}$	$n+ \ n- \text{ PULSE } ( V_1 \ V_2 \ t_d \ t_r \ t_f \ PW \ T )$	Transient
$\begin{Bmatrix} Vname \\ Iname \end{Bmatrix}$	$n+ \ n- \text{ PWL } ( t_1, v_1 \ t_2, v_2 \ \dots \ t_n, v_n )$	Transient



# SDL: Time-Varying Signal Sources

### Time-Varying Signal





### Spice Description

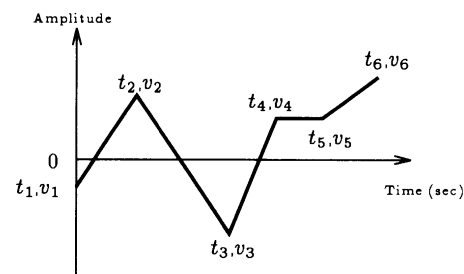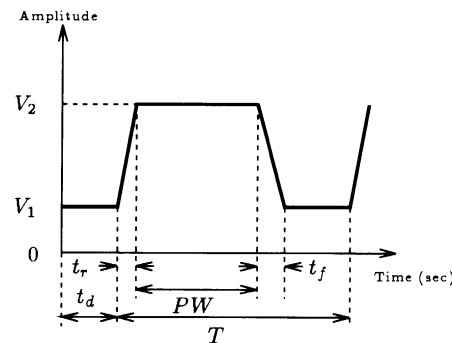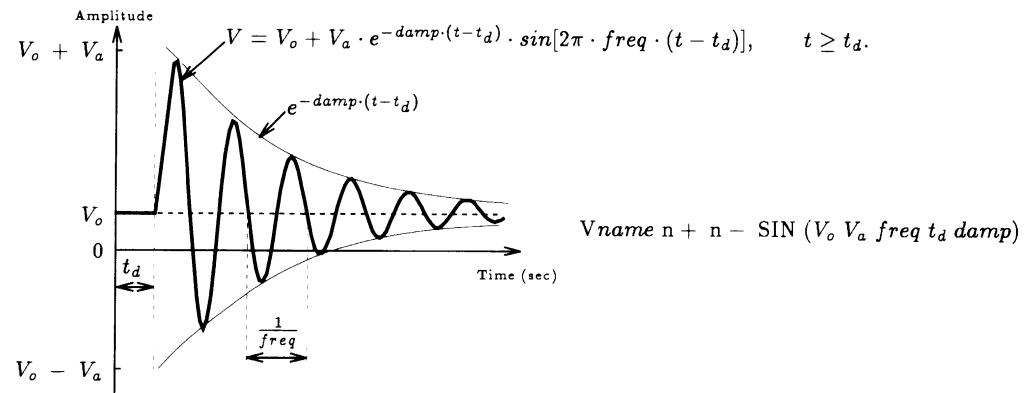



# Spice Description Language: Linear Dependent Sources

## Linear Dependent Sources
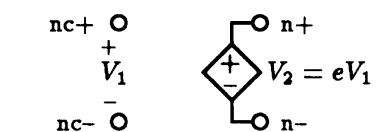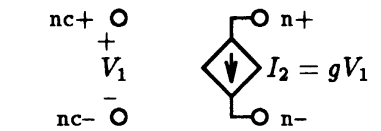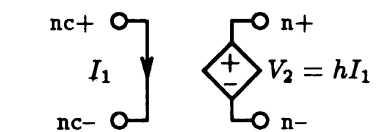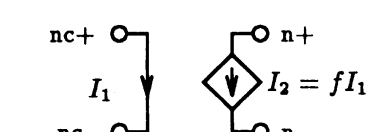
<u>Element</u>	<u>Spice Description</u>
 <p>voltage-controlled voltage source</p>	$Ename\ n+\ n-\ nc+\ nc-\ e\_value$
 <p>voltage-controlled voltage source</p>	$Gname\ n+\ n-\ nc+\ nc-\ g\_value$
 <p>current-controlled voltage source</p>	$Hname\ n+\ n-\ Vname\ h\_value$ $Vname\ nc+\ nc-\ 0$
 <p>current-controlled voltage source</p>	$Fname\ n+\ n-\ Vname\ f\_value$ $Vname\ nc+\ nc-\ 0$

**Figure 1.7** Linear dependent sources. Notice that the CCVS and the CCCS are both specified using two Spice statements, unlike the other two dependent sources.



# Spice Description Language: Main Analysis Commands or Directives

Analysis Requests	Spice Command
Operating-point	.OP
DC sweep	.DC <i>source_name start_value stop_value step_value</i>
AC frequency response	.AC DEC <i>points_per_decade freq_start freq_stop</i> .AC OCT <i>points_per_octave freq_start freq_stop</i> .AC LIN <i>total_points freq_start freq_stop</i>
Transient response	.TRAN <i>time_step time_stop [no_print_time max_step_size] [UIC]</i> .IC <i>V(node<sub>1</sub>) = value V(node<sub>2</sub>) = value . . . .</i>



## Spice Description Language: PSpice Output Requests (Not Used in LTSpice)



Output Requests	Spice Command
Print data points	<code>.PRINT DC <i>output_variables</i></code> <code>.PRINT AC <i>output_variables</i></code> <code>.PRINT TRAN <i>output_variables</i></code>
Plot data points	<code>.PLOT DC <i>output_variables</i> [(<i>lower_plot_limit</i>, <i>upper_plot_limit</i>)]</code> <code>.PLOT AC <i>output_variables</i> [(<i>lower_plot_limit</i>, <i>upper_plot_limit</i>)]</code> <code>.PLOT TRAN <i>output_variables</i> [(<i>lower_plot_limit</i>, <i>upper_plot_limit</i>)]</code>

Notes:

1. Spice *output\_variables* can be a voltage at any node  $V(node)$ , the voltage difference between two nodes  $V(node_1, node_2)$ , or the current through a voltage source  $I(Vname)$ .
2. AC *output\_variables* can also be
  - Vr, Ir: real part
  - Vi, Ii: imaginary part
  - Vm, Im: magnitude
  - Vp, Ip: phase
  - Vdb, IdB: decibels
3. PSpice provides a greater flexibility for specifying *output\_variables*.



# Input /Output To SPICE

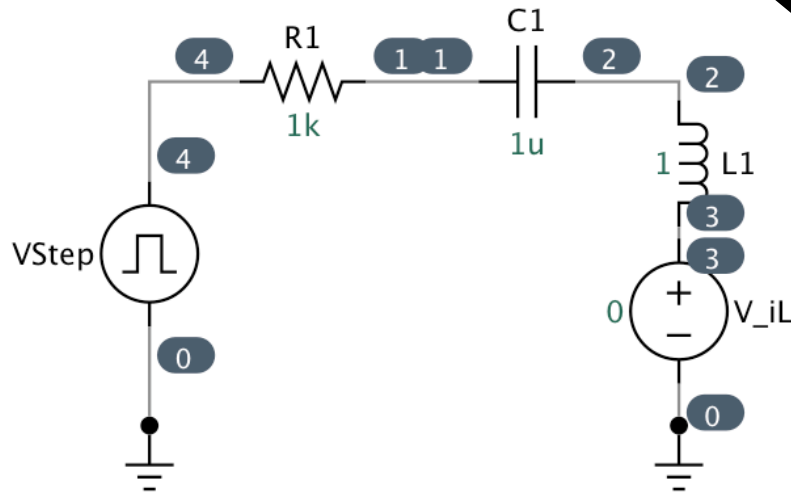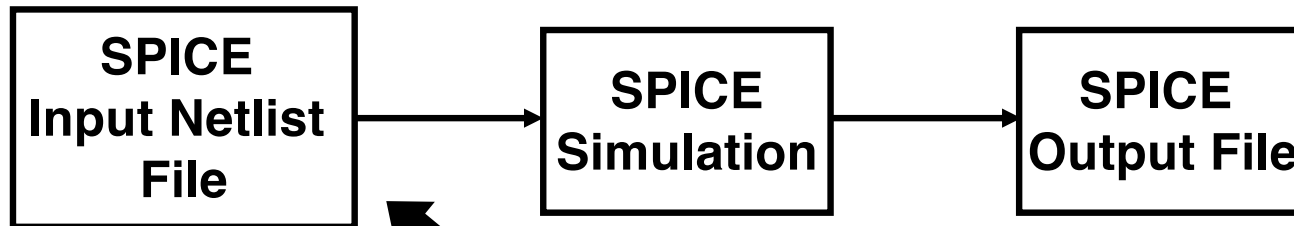

## SPICE Input Netlist File

Title



Circuit Descriptions

Device Models

Analysis Requests



# Input /Output To SPICE

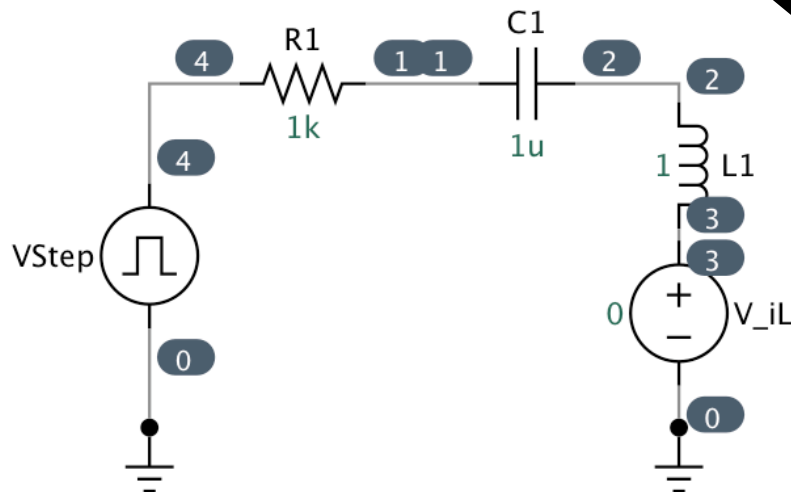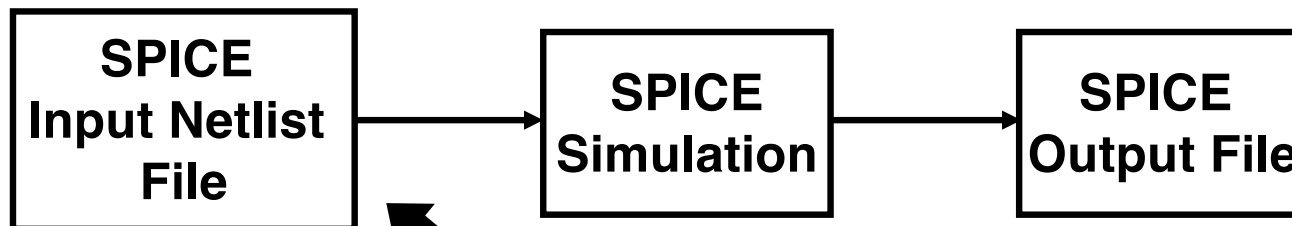


## Spice Input Deck - Derived Directly From Mi-Sugar

```
* 2008-09-30 12:15:59 -0400
* Question P1.17, Roberts & Sedra
*
* Circuit Description
R1 4 1 1k
VStep 4 0 PULSE(0 1 0 10ns 10ns 40m 100ms)
C1 2 1 1u
L1 2 3 1
ViL 3 0 DC 0
*
* Circuit Analysis
.op
.tran 100u 40m 0 100u
.print tran v(1,2) v(2,3) v(3)
.print tran i(ViL)
.end
```




# Input /Output To SPICE

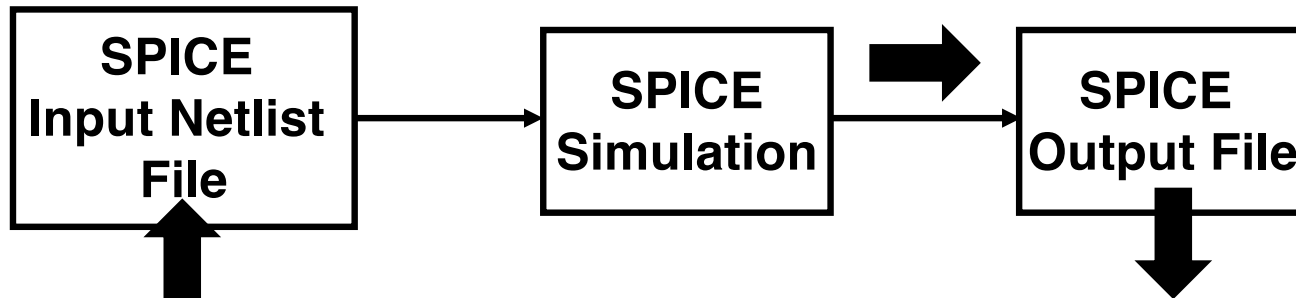


Spice Input Deck - Derived Directly From Mi-Sugar
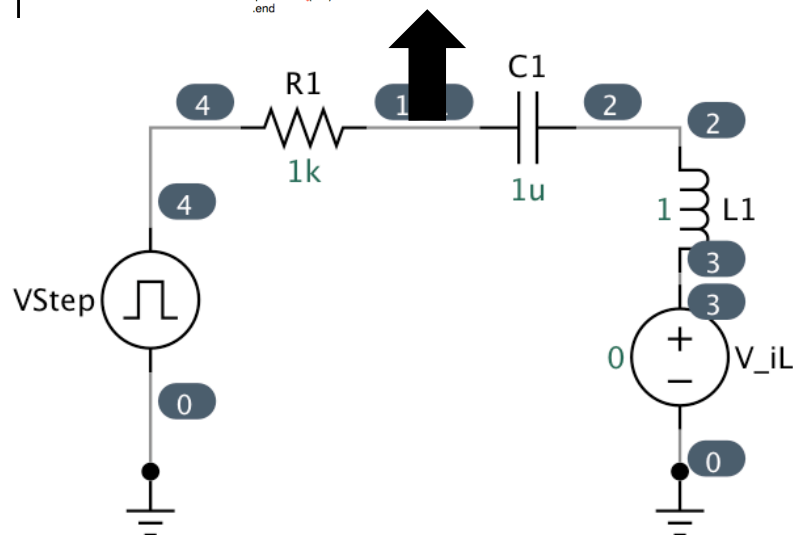
```
* 2008-09-30 12:15:59 -0400
* Question P1.17, Roberts & Sedra
*
* Circuit Description
R1 4 1 1k
VStep 4 0 PULSE(0 1 0 10ns 10ns 40m 100ms)
C1 2 1 1u
L1 2 3 1
VIL 3 0 DC 0
*
* Circuit Analysis
.op
.tran 100u 40m 0 100u
.print tran v(1,2) v(2,3) v(3)
.print tran i(VIL)
.end
```




voltage across resistor R1


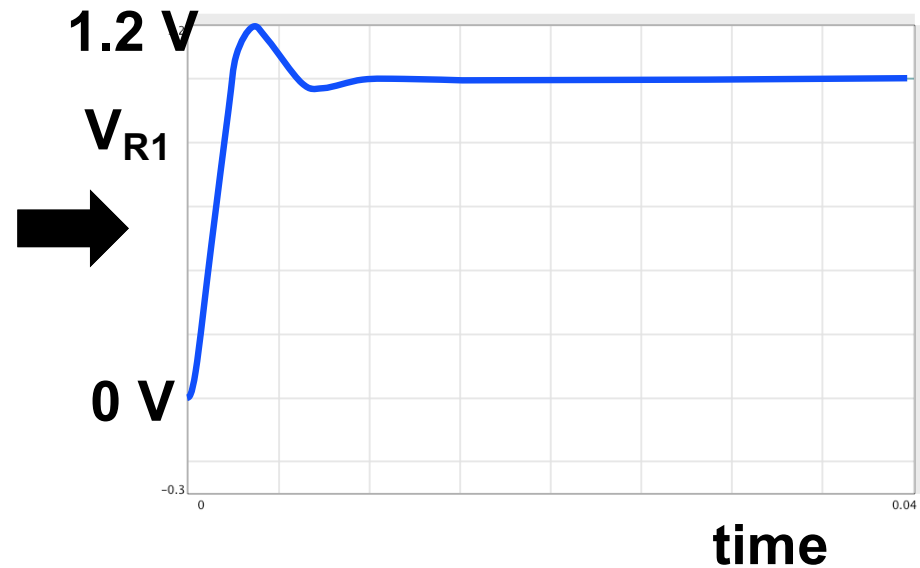




# Input /Output To SPICE

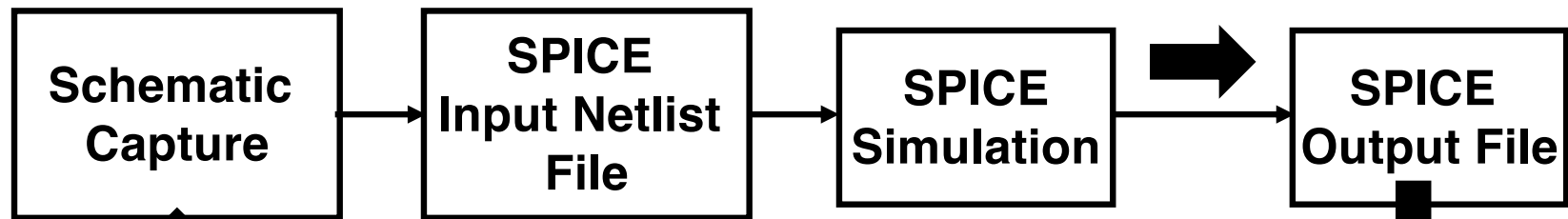

voltage across resistor R1

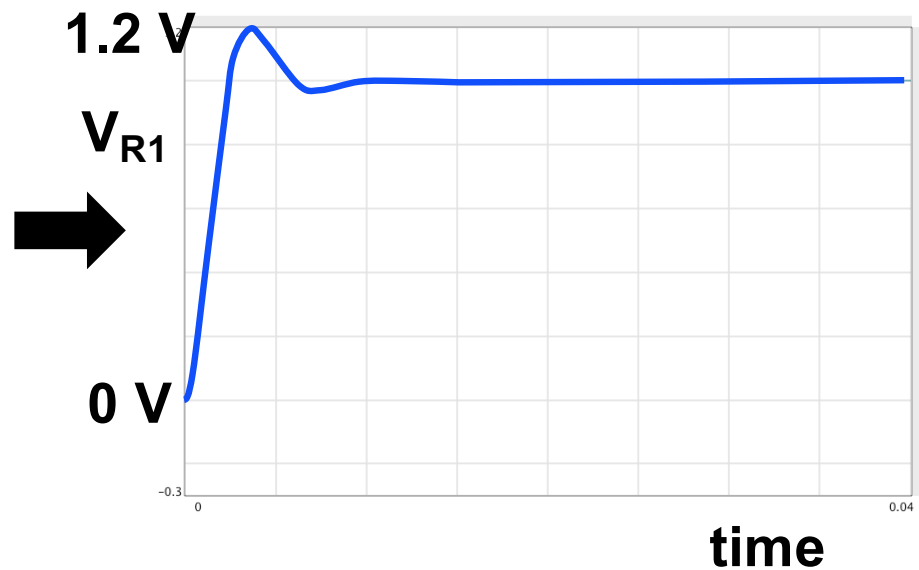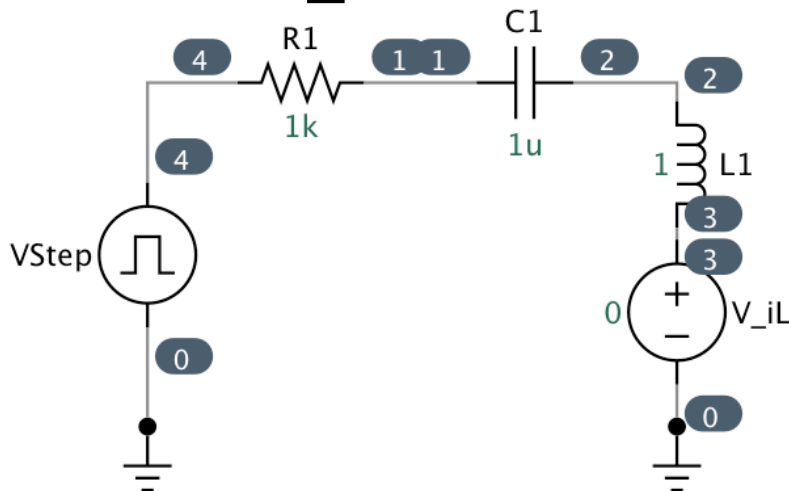



## Outline

- Introduction
- Value of Prototyping
- Analog Simulation
- ➡ Where To Get Spice
- Summary



## Where Do You Get SPICE

- The student will use SPICE extensively in this course.
- Free versions of SPICE can be downloaded directly off the internet.
  - Programs come in two flavors:
    - » Text Entry type
      - Spice3 (windows)
      - MACSpice (OS X)
    - » Schematic Circuit Entry
      - LTSpice
      - PSpice
      - TINA-TI

**Many resources  
on internet but on  
your own**



McGill

304-335

# Course Web Site

Welcome Contact Research Activity Courses My Textbooks

## ECSE 304-335 Microelectronics

### Course Details:

- ▶ [Course Description](#)
- ▶ [Quiz Dates](#)

### Course Support People:

- ▶ [Teaching Assistants](#)
- ▶ [Lab Instructors](#)

### Instructor Material (login required, maybe twice):

- ▶ [Lecture Notes](#)
- ▶ [Animations](#)
- ▶ [Online Spice Resources](#)

### Course Work (login required):

- ▶ [Assignments](#)
- ▶ [Simulation Laboratory](#)

Lecture Notes Animations Assignments Simulation Lab Overview  
Lab Description Midterm Details Final Details

## On-Line Spice Resources

### ▶ My Textbooks on Spice

- [PSpice Reference](#)
- [LTSpice Reference](#)

### ▶ Software Downloads

- [Cadence PSpice](#)
- [Analog Devices](#)

[ECSE 304-335](#)



## Summary

- An introduction to SPICE was given; the student will use SPICE throughout this course.
- The idea of negative feedback was described, and this will come to be the central idea on how to fix many of your circuit impairments.